

Laplacetransform med MATLAB

Til bruk ved kretsanalyse i ELE142

Dette er en rask gjennomgang av funksjoner til bruk for å regne Laplacetransformer i MATLAB med hovedvekt på følgende funksjoner

- laplace Laplacetransform
- ilaplace Invers Laplacetransform
- partfrac Delbrøkoppspalting
- simplify Forenkle uttrykk

Alle eksempler er i gule tekstbokser. For lesbarhetens skyld er unødvendige linjeskift og mellomrom fjernet (med mindre annet er spesifisert). Alle gule tekstbokser forutsetter at vi starter med blanke ark, altså at følgende kommandorekke er utført:

```
>> clear % Sletter gamle variabler
>> clc % Sletter skjermen for gamle utregninger
```

Videre er kommentarer skrevet med grønt, feilmeldinger i rødt og alle svar med blått. Også dette for å øke lesbarheten.

1 Laplacetransform og invers Laplacetransform

Laplacetransformen omformer fra tidsplanet til det komplekse frekvensplanet, bedre kjent som splanet. Denne gjennomgangen tar utgangspunkt i læreboken til Nilsson/Riedel (Electric Circuits, 9th edition), og da spesielt tabell 12.1 samt oppgavene underveis i kapittel 12 og 13, kalt "Assessment Problems".

TABLE 12.1 An Abbreviated List of Laplace Transform Pairs

Туре	$f(t) \ (t>0-)$	F(s)
(impulse)	$\delta(t)$	1
(step)	u(t)	$\frac{1}{s}$
(ramp)	t	$\frac{1}{s^2}$
(exponential)	e^{-at}	$\frac{1}{s+a}$
(sinc)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
(cosine)	cos ωt	$\frac{s}{s^2+\omega^2}$
(damped ramp)	te^{-at}	$\frac{1}{(s+a)^2}$
(damped sine)	$e^{-at}\sin\omega t$	$\frac{\omega}{(s+a)^2+\omega^2}$
(damped cosine)	$e^{-at}\cos\omega t$	$\frac{s+a}{(s+a)^2+\omega^2}$



1.1 Impulsfunksjonen (dirac-funksjonen)

$$f(t) = \delta(t) \leftrightarrow F(s) = 1$$

1.2 Step-funsjonen (Heaviside)

$$f(t) = u(t) \leftrightarrow F(s) = \frac{1}{s}$$

```
>> syms t s % Deklarerer først de nødvendige variablene
>>
>> laplace(heaviside(t)) % Heaviside er det samme som u(t)
    ans = 1/s
>> ilaplace(1/s)
    ans = 1
>> % Legg merkle til at MATLAB ikke skriver u(t)
```

Her må vi selv anta at dette kun gjelder for t > 0 for den inverse Laplacetransformasjonen




1.3 Rampefunksjonen

$$f(t) = t \leftrightarrow F(s) = \frac{1}{s^2}$$

```
>> syms t s
>>
>> laplace(t)
    ans = 1/s^2
>>
>> ilaplace(1/s^2)
    ans = t
```

Både Laplacetransform og invers Laplacetransform gir korrekt svar.

1.4 Eksponentialfunksjonen

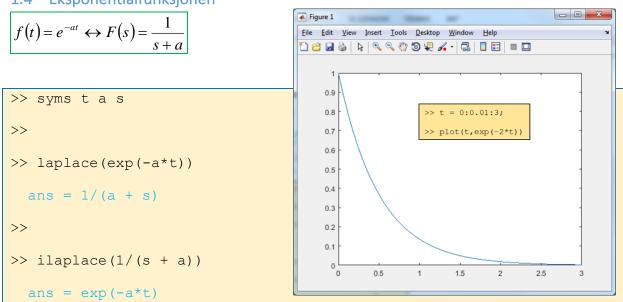

Både Laplacetransform og invers Laplacetransform gir korrekt svar.



1.5 Sinusfunksjonen

$$f(t) = \sin(\omega t) \leftrightarrow F(s) = \frac{\omega}{s^2 + \omega^2}$$

Både Laplacetransform og invers Laplacetransform gir korrekt svar.

1.6 Cosinusfunksjonen

$$f(t) = \cos(\omega t) \leftrightarrow F(s) = \frac{s}{s^2 + \omega^2}$$

```
>> syms t s w
>>
>> laplace(cos(w*t))
   ans = s/(w^2 + s^2)
>>
>> ilaplace(s/(w^2 + s^2))
ans = cos(w*t)
```


Både Laplacetransform og invers Laplacetransform gir korrekt svar.



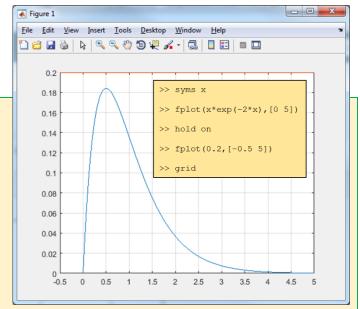1.7 Dempet rampe

$$f(t) = t \cdot e^{-at} \leftrightarrow F(s) = \frac{1}{(s+a)^2}$$

```
>> syms t s a
>>
>> laplace(t*exp(-a*t))
   ans = 1/(a + s)^2
>>
>> ilaplace(1/(a + s)^2)
ans = t*exp(-a*t)
```



Både Laplacetransform og invers Laplacetransform gir korrekt svar.

1.8 Dempet sinus

$$f(t) = e^{-at} \cdot \sin(t) \leftrightarrow F(s) = \frac{\omega}{(s+a)^2 + \omega^2}$$




Både Laplacetransform og invers Laplacetransform gir korrekt svar.



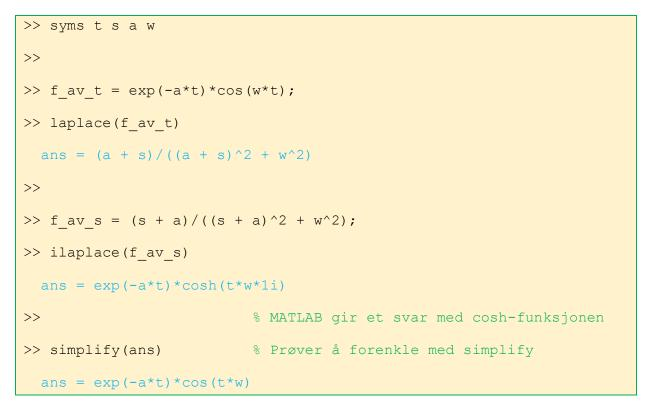1.9 Dempet cosinus

$$f(t) = e^{-at} \cdot \cos(t) \leftrightarrow F(s) = \frac{s+a}{(s+a)^2 + \omega^2}$$



Her ga MATLAB et svar med hyperbolisk cosinus med imaginær operand. Det var nødvendig med en «simplify»-operasjon for å få ønsket svar.



2 Oppgaver med Laplacetransformasjon og invers Laplacetransformasjon

ASSESSMENT PROBLEM

Objective 1—Be able to calculate the Laplace transform of a function using the definition of Laplace transform

12.1 Use the defining integral to


Answer: (a) $s/(s^2 - \beta^2)$;

a) find the Laplace transform of cosh βt;
b) find the Laplace transform of sinh βt.

(b) $\beta/(s^2 - \beta^2)$.

NOTE: Also try Chapter Problem 12.17.

Fra Wikipedia:

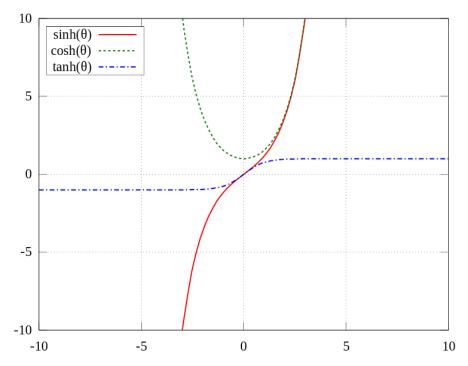

The hyperbolic functions are:

Hyperbolic sine:

$$\sinh x = \frac{e^x - e^{-x}}{2} = \frac{e^{2x} - 1}{2e^x} = \frac{1 - e^{-2x}}{2e^{-x}}$$

· Hyperbolic cosine:

$$\cosh x = \frac{e^x + e^{-x}}{2} = \frac{e^{2x} + 1}{2e^x} = \frac{1 + e^{-2x}}{2e^{-x}}$$

· Hyperbolic tangent:

$$\tanh x = \frac{\sinh x}{\cosh x} = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{e^{2x} - 1}{e^{2x} + 1} = \frac{1 - e^{-2x}}{1 + e^{-2x}}$$



```
% B skal symbolisere beta
>> syms B s t
>>
                                        % Prøver med cosh direkte
>> laplace(cosh(B*t))
 ans = -s/(B^2 - s^2)
>>
                                        % OK i henhold til fasit
>> laplace((exp(B*t)+exp(-B*t))/2) % Prøver utvidet variant
ans = 1/(2*(B + s)) - 1/(2*(B - s))
>>
                                        % Samme som ovenfor?
>> simplify(ans)
                                        % Prøver forenkling
ans = -s/(B^2 - s^2)
                                        % OK i henhold til fasit
>>
>>
>> laplace(sinh(B*t))
ans = -B/(B^2 - s^2)
>>
                                       % OK i henhold til fasit
>> laplace((exp(B*t)-exp(-B*t))/2) % Prøver utvidet variant
 ans = -1/(2*(B + s)) - 1/(2*(B - s))
>>
                                        % Samme som ovenfor?
>> simplify(ans)
                                        % Prøver forenkling
  ans = -B/(B^2 - s^2)
                                        % OK i henhold til fasit
>>
```

Legg merke til at det noen ganger er nødvendig å bruke simplify-funksjonen



Objective 1—Be able to calculate the Laplace transform of a function using the Laplace transform table or a table of operational transforms

12.2 Use the appropriate operational transform from Table 12.2 to find the Laplace transform of each function:

of each function:
a)
$$t^2e^{-at}$$
;

b)
$$\frac{d}{dt}(e^{-at}\sinh\beta t)$$
;

c) $t \cos \omega t$.

NOTE: Also try Chapter Problems 11.14 and 11.22.

Answer: (a)
$$\frac{2}{(s+a)^3}$$
;

(b)
$$\frac{\beta s}{(s+a)^2 - \beta^2};$$

(c)
$$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$$

```
>> % Oppgave 12.2.a
>> syms t a B w s
>> laplace(t^2*exp(-a*t))
  ans = 2/(a + s)^3
>> % Denne stemmer rett fram med fasit
>>
>> % Oppgave 12.2.b
>> laplace(diff(exp(-a*t)*sinh(B*t)))
  ans = (B*(a + s))/((a + s)^2 - B^2) - (B*a)/((a + s)^2 - B^2)
>> simplify(ans)
  ans = (B*s)/(-B^2 + a^2 + 2*a*s + s^2)
>> % Denne måtte ryddes med "simplyfy".
>> % Svaret er ikke helt i mål, første kvadratsetning gir rett svar
>>
>> % Oppgave 12.2.c
>> laplace(t*cos(w*t))
  ans = (2*s^2)/(s^2 + w^2)^2 - 1/(s^2 + w^2)
>> simplify(ans)
  ans = (s^2 - w^2)/(s^2 + w^2)^2
>> % Denne stemmer rett fram med fasit
```



Objective 2—Be able to calculate the inverse Laplace transform using partial fraction expansion and the Laplace transform table

12.3 Find
$$f(t)$$
 if
$$F(s) = \frac{6s^2 + 26s + 26}{(s+1)(s+2)(s+3)}.$$
 Answer: $f(t) = (3e^{-t} + 2e^{-2t} + e^{-3t})u(t).$

```
>> syms s t
>> ilaplace((6*s^2+26*s+26)/((s+1)*(s+2)*(s+3)))
ans = 3*exp(-t) + 2*exp(-2*t) + exp(-3*t)
```

Dette ser ut til å stemme ganske bra med fasit, men ikke glem u(t). Dette gjelder altså når t > 0.

Vi kan se mer på detaljene ved å delbrøkoppspalte:

```
>> syms s t
>> funksjon = (6*s^2+26*s+26)/((s+1)*(s+2)*(s+3));
>> partfrac(funksjon)
ans = 3/(s + 1) + 2/(s + 2) + 1/(s + 3)
>> ilaplace(ans)
ans = 3*exp(-t) + 2*exp(-2*t) + exp(-3*t)
```

Altså:
$$F(s) = \frac{6s^2 + 26s + 26}{(s+1)(s+2)(s+3)} = \frac{3}{s+1} + \frac{2}{s+2} + \frac{1}{s+3} \longleftrightarrow f(t) = \left[3e^{-t} + 2e^{-2t} + e^{-3t}\right] \cdot u(t)$$

Legg nok en gang merke til at ilaplace-funksjonen ikke tar med u(t).



Objective 2—Be able to calculate the inverse Laplace transform using partial fraction expansion and the Laplace transform table

12.4 Find
$$f(t)$$
 if
$$F(s) = \frac{7s^2 + 63s + 134}{(s+3)(s+4)(s+5)}.$$
Answer: $f(t) = (4e^{-3t} + 6e^{-4t} - 3e^{-5t})u(t)$.

```
>> syms s t
>> ilaplace((7*s^2+63*s+134)/((s+3)*(s+4)*(s+5)))
    ans = 4*exp(-3*t) + 6*exp(-4*t) 3 exp(-5*t)
>>
>> % Går veien om "partfrac" for å vise detaljene
>> funksjon = (7*s^2+63*s+134)/((s+3)*(s+4)*(s+5));
>> partfrac(funksjon)
    ans = 4/(s+3) + 6/(s+4) - 3/(s+5)
>> ilaplace(ans)
    ans = 4*exp(-3*t) + 6*exp(-4*t) - 3*exp(-5*t)
```

Stemmer bra med fasit.

ASSESSMENT PROBLEM

Objective 2—Be able to calculate the inverse Laplace transform using partial fraction expansion and the Laplace transform table

```
12.5 Find f(t) if Answer: f(t) = (10e^{-5t} - 8.33e^{-5t} \sin 12t)u(t).

F(s) = \frac{10(s^2 + 119)}{(s+5)(s^2 + 10s + 169)}.
```

```
>> syms s t
>> funksjon = 10*(s^2 + 119)/((s + 5)*(s^2 + 10*s + 169));
>> partfrac(funksjon)
   ans = 10/(s + 5) - 100/(s^2 + 10*s + 169)
>> ilaplace(ans)
   ans = 10*exp(-5*t) - (25*sin(12*t)*exp(-5*t))/3
```



Objective 2—Be able to calculate the inverse Laplace transform using partial fraction expansion and the Laplace transform table

12.6 Find
$$f(t)$$
 if Answer: $f(t) = (1 + 2te^{-t} + 3e^{-t})u(t)$.

$$F(s) = \frac{(4s^2 + 7s + 1)}{s(s + 1)^2}$$

```
>> syms s t
>> funksjon = (4*s^2 + 7*s + 1)/(s*(s + 1)^2);
>> partfrac(funksjon)
ans = 3/(s + 1) + 2/(s + 1)^2 + 1/s
>> ilaplace(ans)
ans = 3*exp(-t) + 2*t*exp(-t) + 1
```

Stemmer bra med fasit.

ASSESSMENT PROBLEM

Objective 2—Be able to calculate the inverse Laplace transform using partial fraction expansion and the Laplace transform table

12.7 Find
$$f(t)$$
 if Answer: $f(t) = (-20te^{-2t}\cos t + 20e^{-2t}\sin t)u(t)$.
$$F(s) = \frac{40}{(s^2 + 4s + 5)^2}$$

```
>> syms s t
>> funksjon = 40/(s^2+4*s+5)^2;
>> ilaplace(funksjon)
    ans = 20*exp(-2*t)*sin(t) - 10*t*(exp(-2*t)*cos(t) + exp(-2*t)*sin(t)*1i) - 10*t*(exp(-2*t)*cos(t) - exp(-2*t)*sin(t)*1i)
>> % Dette så ikke så pent ut. Prøver å rydde
>> simplify(ans)
    ans = 20*exp(-2*t)*(sin(t) - t*cos(t))
```

Stemmer bra med fasit.



12.8 Find
$$f(t)$$
 if
$$F(s) = \frac{(5s^2 + 29s + 32)}{(s+2)(s+4)}.$$
Answer: $f(t) = 5\delta(t) - (3e^{-2t} - 2e^{-4t})u(t).$

```
>> syms t s
>> funksjon = (5*s^2 + 29*s + 32)/((s + 2)*(s + 4));
>> partfrac(funksjon)
ans = 2/(s + 4) - 3/(s + 2) + 5
>> ilaplace(funksjon)
ans = 2*exp(-4*t) - 3*exp(-2*t) + 5*dirac(t)
```

Stemmer bra med fasit



```
12.9 Find f(t) if
F(s) = \frac{(2s^3 + 8s^2 + 2s - 4)}{(s^2 + 5s + 4)}.
Answer: f(t) = 2\frac{d\delta(t)}{dt} - 2\delta(t) + 4e^{-4t}u(t).
```

```
>> syms t s
>> funksjon = (2*s^3 + 8*s^2 + 2*s - 4)/(s^2 + 5*s + 4);
>> partfrac(funksjon)
   ans = 2*s + 4/(s + 4) - 2
>> ilaplace(ans)
   ans = 4*exp(-4*t) - 2*dirac(t) + 2*dirac(1, t)
```

Fra hjelpesiden til dirac-funksjonen:

Description

dirac(x) represents the Dirac delta function of x.

dirac(n,x) represents the nth derivative of the Dirac delta function at x.

Det betyr at 2*dirac(1, t) er det samme som $2 \cdot \frac{d\delta(t)}{dt}$. Tester dette:

```
>> syms s t
>> funksjon = 4*exp(-4*t) - 2*dirac(t) + 2*diff(dirac(t));
>> laplace(funksjon)
ans = 2*s + 4/(s + 4) - 2
```

Dette er det samme som etter delbrøkoppspaltinga ovenfor.



Objective 3—Understand and know how to use the initial value theorem and the final value theorem

12.10 Use the initial- and final-value theorems to find Answer: 7, 0; 4, 1; and 0, 0. the initial and final values of f(t) in Assessment Problems 12.4, 12.6, and 12.7.

12.4 Find f(t) if

12.6 Find
$$f(t)$$
 if

12.6 Find
$$f(t)$$
 if 12.7 Find $f(t)$ if

$$F(s) = \frac{7s^2 + 63s + 134}{(s+3)(s+4)(s+5)}. \quad F(s) = \frac{(4s^2 + 7s + 1)}{s(s+1)^2}. \quad F(s) = \frac{40}{(s^2 + 4s + 5)^2}.$$

$$F(s) = \frac{(4s^2 + 7s + 1)}{s(s + 1)^2}$$

$$F(s) = \frac{40}{(s^2 + 4s + 5)^2}.$$

Start- og sluttverditeoremet sier at:

$$\lim_{t\to 0^+} f(t) = \lim_{s\to \infty} sF(s),$$

(12.93) ◀ Initial value theorem

$$\lim_{t\to\infty} f(t) = \lim_{s\to 0} sF(s).$$

(12.94) ◀ Final value theorem

```
>> % Fra oppgave 12.4
>> syms s t
\Rightarrow oppg 12 4 = (7*s^2 + 63*s + 134)/((s + 3)*(s + 4)*(s + 5));
>>
>> limit(s*oppg 12 4,s,0)
                                       % s*F(s) når s -> null
 ans = 0
>> limit(ilaplace(oppg_12_4),t,Inf) % f(t) når t -> uendelig
 ans = 0
>>
                                        % Samme svar, alt OK
>>
>> limit(s*oppg 12 4,s,Inf)
                                       % s*F(s) når s -> uendelig
 ans = 7
>> limit(ilaplace(oppg_12_4),t,0) % f(t) når t -> null
  ans = 7
                                        % Samme svar, alt OK
>>
```



```
>> % Fra oppgave 12.6
>> syms s t;
\Rightarrow oppg 12 6 = (4*s^2 + 7*s + 1)/(s*(s + 1)^2);
>>
>> limit(s*oppg 12 6,s,Inf) % Startverdi i s-planet
ans = 4
>> limit(ilaplace(oppg_12_6),t,0) % Startverdi i tidsplanet
ans = 4
>>
>> limit(s*oppg_12_6,s,0) ) % Sluttverdi i s-planet
ans = 1
>> limit(ilaplace(oppg 12 6),t,Inf) % Sluttverdi i tidsplanet
ans = 1
>>
>> % Fra oppgave 12.7
\Rightarrow oppg 12 7 = 40/(s^2+4*s+5)^2;
>>
>> limit(s*oppg 12 7,s,Inf) % Startverdi i s-planet
ans = 0
>> limit(ilaplace(oppg_12_7),t,0) % Startverdi i tidsplanet
ans = 0
>>
>> limit(s*oppg 12 7,s,0) % Sluttverdi i s-planet
ans = 0
>> limit(ilaplace(oppg 12 7),t,Inf) % Sluttverdi i tidsplanet
 ans = 0
```




3 Kretseksempler med Laplace

ASSESSMENT PROBLEMS

Objective 1—Be able to transform a circuit into the s domain using Laplace transforms

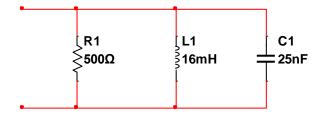- 13.1 A 500 Ω resistor, a 16 mH inductor, and a 25 nF capacitor are connected in parallel.
 - Express the admittance of this parallel combination of elements as a rational function of s.
 - b) Compute the numerical values of the zeros and poles.

Answer: (a)
$$25 \times 10^{-9} (s^2 + 80,000s + 25 \times 10^8)/s$$
;
(b) $-z_1 = -40,000 - j30,000$;
 $-z_2 = -40,000 + j30,000$; $p_1 = 0$.



$$Y = \frac{1}{R} + \frac{1}{sL} + sC = \frac{1}{500} + \frac{1}{s \cdot 16m} + s \cdot 25n$$

```
>> syms s
>> R = 500;
>> L = 16e-3;
>> C = 25e-9;
>> Y = 1/R + 1/(s*L) + s*C
  Y = (944473296573929*s)/37778931862957161709568 + 125/(2*s) +
1/500
>>
                        % MATLAB får avrundingsfeil på heltallsform
\gg Y = vpa(Y, 10)
                       % Variable Precision Arithmetic = avrunding
  Y = 0.000000025 *s + 62.5/s + 0.002
>> Y = collect(Y)
                      % Collect = få uttrykket på felles nevner
  Y = (499999999999999997737405591294313.0*s^2 +
4.00000000000000000019515639104739e36*s + 1.25e41)/(2.0e39*s)
\gg Y = vpa(Y,10)
  Y = (5.0e-40*(5.0e31*s^2 + 4.0e36*s + 1.25e41))/s
>> Y = combine(Y)
                       % Slå sammen parenteser
  Y = (0.00000002499999999999999998885287721112507*s^2 +
0.0020000000000000000002302575992465*s +
62.500000000000000041462313663375)/s
\gg Y = vpa(Y,10)
Y = (0.000000025*s^2 + 0.002*s + 62.5)/s
```

Eksempelet ovenfor ble ikke særlig vakkert på grunn av avrundingsproblematikk. Det er bedre om vi «hjelper» MATLAB og setter opp uttrykket med kun positive tierpotenser (neste side)



$$Y = \frac{1}{R} + \frac{1}{sL} + sC = \frac{1}{500} + \frac{1}{s \cdot 16m} + s \cdot 25n = \frac{1}{500} + \frac{62.5}{s} + \frac{s}{40 \times 10^6} = \frac{1}{500} + \frac{125}{2s} + \frac{s}{40 \times 10^6}$$

```
>> syms s
>> Y = 1/500 + 125/(2*s) + s/40e6
 Y = s/40000000 + 125/(2*s) + 1/500
                    % For å få uttrykket på felles nevner
>> Y = collect(Y)
Y = (s^2 + 80000*s + 2500000000) / (40000000*s)
                   % For å få rydde i uttrykket
>> Y = combine(Y)
 Y = (s^2/40000000 + s/500 + 125/2)/s
                         % For å få vise Y på en vakker måte
>> pretty(Y)
   2
4000000 500 2
>>
>> % Oppgave b er å finne nullpunkter og poler til impedansen
>> Z = inv(Y);
>> poler = solve(1/Z, s)
poler = - 40000 - 30000i
          - 40000 + 30000i
>> nullpunkter = solve(Z)
nullpunkter = 0
```

Dette stemmer bra med fasit.




Objective 1—Be able to transform a circuit into the s domain using Laplace transforms

- 13.2 The parallel circuit in Assessment Problem 13.1 is placed in series with a 2000 Ω resistor.
 - Express the impedance of this series combination as a rational function of s.
 - b) Compute the numerical values of the zeros and poles.

Answer: (a) $2000(s + 50,000)^2/(s^2 + 80,000s + 25 \times 10^8)$;

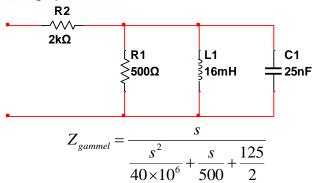(b)
$$-z_1 = -z_2 = -50,000;$$

 $-p_1 = -40,000 - j30,000,$
 $-p_2 = -40,000 + j30,000.$



```
>> syms s
>> Z gammel=s/(s^2/40e6 + s/500 + 125/2);
>> Z ny = Z gammel + 2000;
>> Z ny = collect(Z ny);
                             % Felles nevner
>> pretty(Z ny)
2000 s + 200000000 s + 5000000000000
     s + 80000 s + 2500000000
>> Z ny = simplify(Z ny);
                               % Forenkle uttrykket
>> pretty(Z_ny)
    2000 (s + 50000)
s + 80000 s + 2500000000
>>
>> % Oppgave b, finn poler og nullpunkter
>> nullpunkter = solve(Z ny, s)
 nullpunkter = -50000
                -50000
>> poler = solve(1/Z ny, s)
 poler = - 40000 - 30000i
         - 40000 + 30000i
```




Objective 2—Know how to analyze a circuit in the s domain and be able to transform an s domain solution to the time domain


- 13.3 The switch in the circuit shown has been in position a for a long time. At t = 0, the switch is thrown to position b.
 - a) Find I, V₁, and V₂ as rational functions of s.
 - Find the time-domain expressions for i, v₁, and v₂.

Answer: (a)
$$I = 0.02/(s + 1250)$$
,
 $V_1 = 80/(s + 1250)$,
 $V_2 = 20/(s + 1250)$;

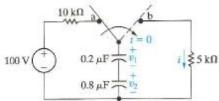(b)
$$i = 20e^{-1250t}u(t)$$
 mA,
 $v_1 = 80e^{-1250t}u(t)$ V,
 $v_2 = 20e^{-1250t}u(t)$ V.



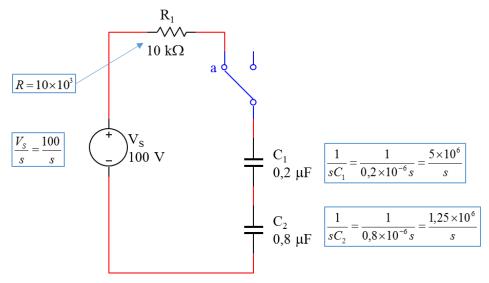
Må først finne spenninga til kondensatorene når de er fullt oppladet. Etter lang tid i posisjon a:



```
>> syms s
>> Z_R1 = 10e3;
>> Z_C1 = 5e6/s;
>> Z_C2 = 1.25e6/s;
>> VS = 100/s;
>> V1 = VS*(Z_C1/(Z_R1 + Z_C1 + Z_C2));  % Spenningsdeling
>> V1_oppladet = limit(s*V1,s,0)  % Sluttverditeoremet
    V1_oppladet = 80
>> V2 = VS*(Z_C2/(Z_R1 + Z_C1 + Z_C2));  % Spenningsdeling
>> V2_oppladet = limit(s*V2,s,0)  % Sluttverditeoremet
    V2_oppladet = 20
```



Etter at bryteren svitsjer over:

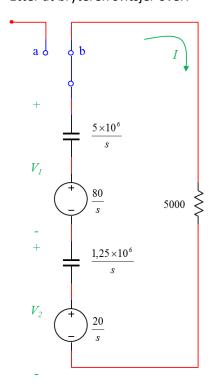

MATLAB-koden blir:

```
>> syms s

>> I = (80/s + 20/s)/(1.25e6/s + 5e6/s + 5000)

I = 100/(s*(6250000/s + 5000))

>> I = simplify(I)

I = 1/(50*(s + 1250))

>> V1 = 80/s - I*5e6/s

V1 = 80/s - 100000/(s*(s + 1250))

>> V1 = collect(V1)

V1 = 80/(s + 1250)

>> V2 = 20/s - I*1.25e6/s

V2 = 20/s - 25000/(s*(s + 1250))

>> V2 = collect(V2)

V2 = 20/(s + 1250)
```

Dette stemmer bra med fasit.



Objective 2—Know how to analyze a circuit in the s domain and be able to transform an s domain solution to the time domain

- 13.4 The energy stored in the circuit shown is zero at the time when the switch is closed.
 - a) Find the s-domain expression for I.
 - Find the time-domain expression for i when t > 0.
 - c) Find the s-domain expression for V.
 - d) Find the time-domain expression for v when t > 0.

```
>> % Oppgave a
>> syms s
>> I = (160/s)/(4.8 + 4*s + 1/(0.25*s))
  I = 160/(s*(4*s + 4/s + 24/5))
>> I = simplify(I)
                                      % For å forenkle uttrykket
  I = 200/(5*s^2 + 6*s + 5)
>> % Oppgave b
>> i av t = ilaplace(I)
  i \text{ av } t = 50*\sin((4*t)/5)*\exp(-(3*t)/5)
>> vpa(i av t, 5)
                                       % Ønsker uttrykket på desimalform
  ans = 50.0*\exp(-0.6*t)*\sin(0.8*t)
>> % Oppgave c
>> V = I*4*s
  V = (800*s)/(5*s^2 + 6*s + 5)
>> % Oppgave d
>> v av t = ilaplace(V)
  v = 160*exp(-(3*t)/5)*(cos((4*t)/5) - (3*sin((4*t)/5))/4)
>> vpa(ans, 5)
  ans = 160.0 \times \exp(-0.6 \times t) \times (\cos(0.8 \times t) - 0.75 \times \sin(0.8 \times t))
```


Svaret på oppgave d er ikke identisk med fasit, men følgende regel kan vise at svaret stemmer:


$$\cos(a+b) = \cos(a) \cdot \cos(b) - \sin(a) \cdot \sin(b)$$




Objective 2—Know how to analyze a circuit in the s domain and be able to transform an s domain solution to the time domain

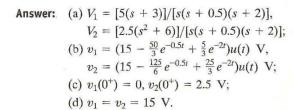- 13.5 The dc current and voltage sources are applied simultaneously to the circuit shown. No energy is stored in the circuit at the instant of application.
 - a) Derive the s-domain expressions for V_1 and V_2 .
 - b) For t > 0, derive the time-domain expressions for v_1 and v_2 .
 - c) Calculate $v_1(0^+)$ and $v_2(0^+)$.
 - d) Compute the steady-state values of v_1 and v_2 .



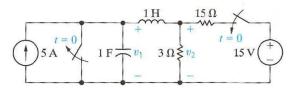

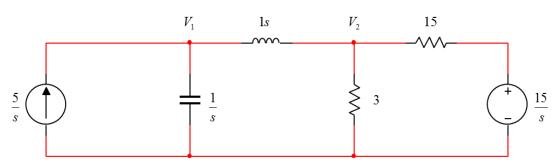



Fortsetter med de samme variablene (uten å ha slettet med en CLEAR)

```
% Sjekker hvordan V1 ser ut i minnet
>> V1
 V1 = (10*(s + 3))/(s*(2*s^2 + 5*s + 2))
>> V2
                               % Sjekker hvordan V2 ser ut i minnet
 V2 = (5*(s^2 + 6))/(s*(2*s^2 + 5*s + 2))
>> % Oppgave b
>> v1 = ilaplace(V1)
 v1 = (5*exp(-2*t))/3 - (50*exp(-t/2))/3 + 15
>> v2 = ilaplace(V2)
 v2 = (25*exp(-2*t))/3 - (125*exp(-t/2))/6 + 15
>>
>> % Oppgave c
>> v1_null_pluss = limit(s*V1,s,inf) % Bruker startverditeoremet
 v1 \text{ null pluss} = 0
>> v2 null pluss = limit(s*V2,s,inf) % Bruker startverditeoremet
 v2 null pluss = 5/2
>>
>> % Oppgave d
>> v2 ss = limit(s*V2,s,0) % Bruker sluttverditeoremet
v2 ss = 15
>> v1 ss = limit(s*V1,s,0)
                               % Bruker sluttverditeoremet
 v1 ss = 15
```

Fasit og MATLAB stemmer overens




Objective 2—Know how to analyze a circuit in the s domain and be able to transform an s-domain solution to the time domain

- 13.6 The initial charge on the capacitor in the circuit shown is zero.
 - a) Find the s-domain Thévenin equivalent circuit with respect to terminals a and b.
 - Find the s-domain expression for the current that the circuit delivers to a load consisting of a 1 H inductor in series with a 2 Ω resistor.

Answer: (a)
$$V_{\text{Tb}} = V_{\text{ab}} = [20(s+2.4)]/[s(s+2)],$$


 $Z_{\text{Th}} = 5(s+2.8)/(s+2);$

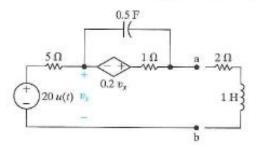(b)
$$I_{ab} = [20(s+2.4)]/[s(s+3)(s+6)].$$



Oppgave a

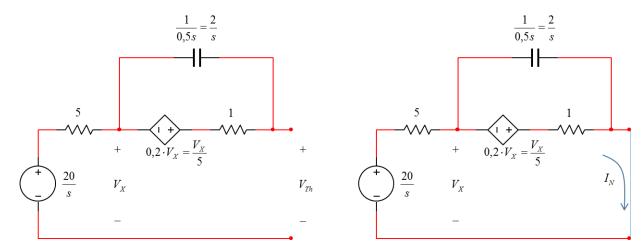Må først tegne kretsen i s-planet med mål om å finne Thevenin-ekvivalenten:



```
>> Oppgave a
>> syms s Vx Vth In Zth
>> % Først finne Theveninspenninga (venstre figur)
>> likn1 = Vx - 20/s == 0;
>> likn2 = (Vth - Vx)/(2/s) - ((Vx + Vx/5) - Vth)/1 == 0;
>> svar = solve([likn1 likn2] , [Vx Vth]);
>> Vth = svar.Vth
    Vth = (4*(5*s + 12))/(s*(s + 2))
>> % Fortsetter på neste side
```






Oppgave b

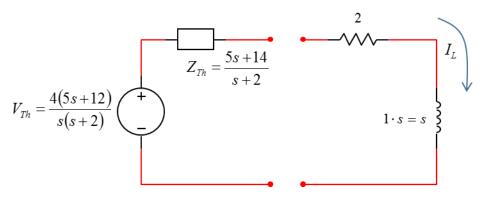b) Find the s-domain expression for the current that the circuit delivers to a load consisting of a 1 H inductor in series with a 2 Ω resistor.

Erstatter kretsen med Thevenin-ekvivalenten:



```
>> % Fortsetter fra tidligere
>> Vth
                                        % Sjekker Theveninspenningen
 Vth = (4*(5*s + 12))/(s*(s + 2))
>> Zth
                                       % Sjekker Theveninimpedansen
  Zth = (5*s + 14)/(s + 2)
>> syms IL
                                       % Må legge til en ny variabel
>> IL = Vth/(Zth + 2 + s)
  IL = (4*(5*s + 12))/(s*(s + 2)*(s + (5*s + 14)/(s + 2) + 2))
>> IL = simplify(IL)
  IL = (20*s + 48)/(s*(s^2 + 9*s + 18))
>> poles(IL)
                    % Sjekker om løsninga har samme poler som fasit
  ans = -3
        -6
         0
>> % Fasit stemmer overens med MATLAB
```